

Half Adder Component

	B/		
	0	1	
A/	0	1	sum/
	1	0	





{[A/0, B/0], [A/1, B/1]} -> sum/0;
 {[A/1, B/0], [A/0, B/1]} -> sum/1;

	B/		
	0	1	
A/	0	0	carry/
	1	1	

{[A/0, B/0], [A/1, B/0], [A/0, B/1]} -> carryout/0;
 [A/1, B/1] -> carryout/1;

Symbolic specification

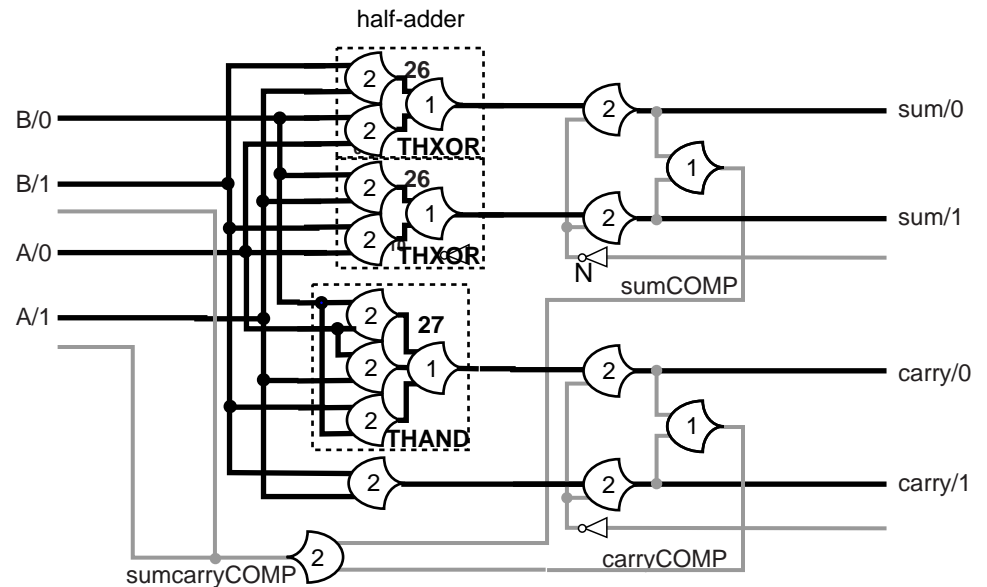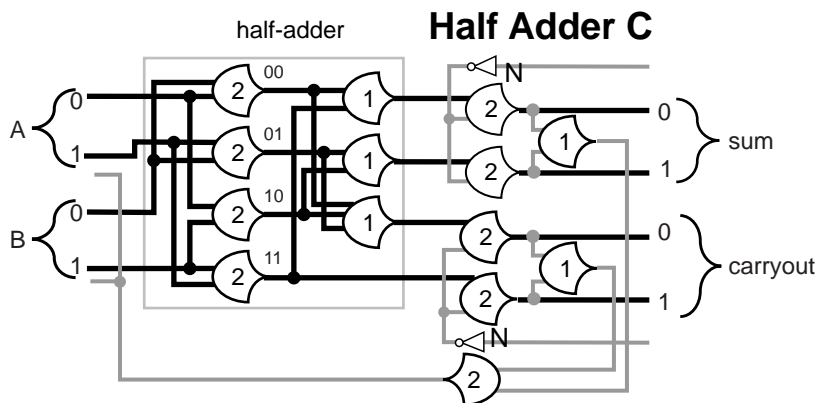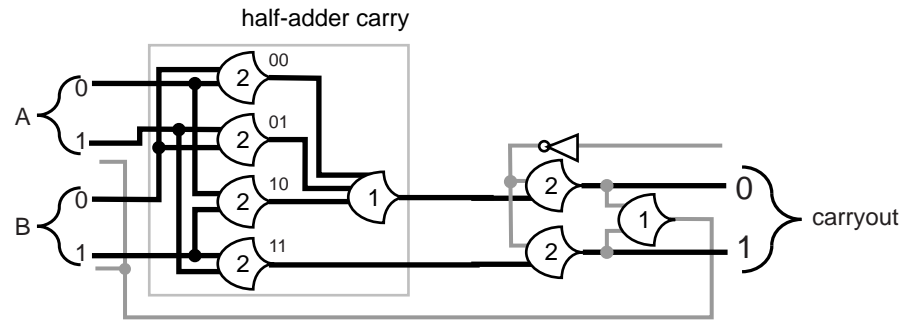 
```
// specify the half add component
halfadd(A, B -> sum, carryout){
flow [A, B] -> [sum, carryout];
token {0:1} A, B, sum, carryout;
    {[A/0, B/0], [A/1, B/1]} -> sum/0;
    {[A/1, B/0], [A/0, B/1]} -> sum/1;
    {[A/0, B/0], [A/1, B/0], [A/0, B/1]} -> carryout/0;
    [A/1, B/1] -> carryout/1;
close A <- [sum/#, carryout/#];
close B <- [sum/#, carryout/#];
}
```



input incompleteness for carry


Given two output flow paths of a single shared completeness behavior If the completeness of transition one output flow implies the completeness of transition of the input flow then the other output flow need not imply the completeness of input but only the completeness of propagation and the correctness of the output. The AND of the completeness of the two output flows closes with the input and fulfills the completeness criterion

 In the case of the half adder the sum implies the completeness of the input so the carry can be generated with partial input. Specifically, if $A/0$ then $carry/0$ and it is not necessary to wait on B to generate the carry. In the case of the counter B will be the carryin from the lower order digit. So to generate carryout half the time we will not have to wait on carryin.



Half Adder A

 The carry orphan causes a wait for the null carry ripple





Half Adder B

The carry orphan does not cause a wait for the null carry ripple

Composing the half adder ring

initialize data wavefront

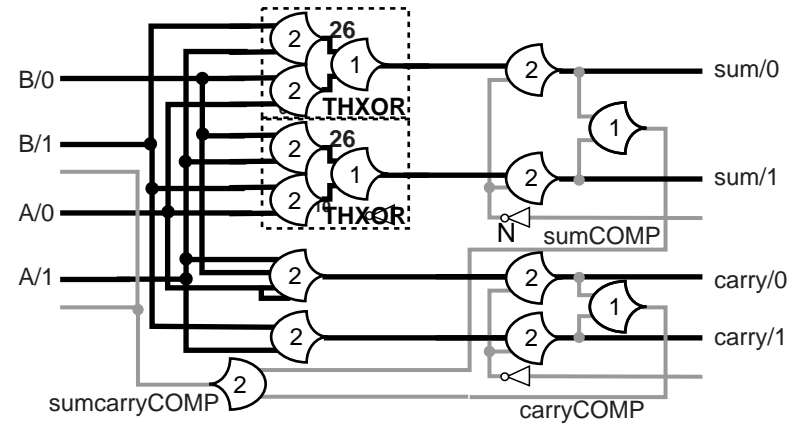 


halfaddA component

halfadd(B, carryin -> count, carryout)

Symbolic specification

```
// compose the digit halfadd ring
digit_count(carryin -> carryout, count){
flow carryin -> [count, carryout];
token {0:1} carryin, carryout, count, B, D, A(0);
  halfadd(B, carryin -> count, carryout)
  (count -> D);
  (D -> A);
  (A -> B);
close carryin <- {carryout/#, count/#};
close count <- [D/#, ?/#];
close carryout <- ?/#;
}
```

halfadd ring counter component

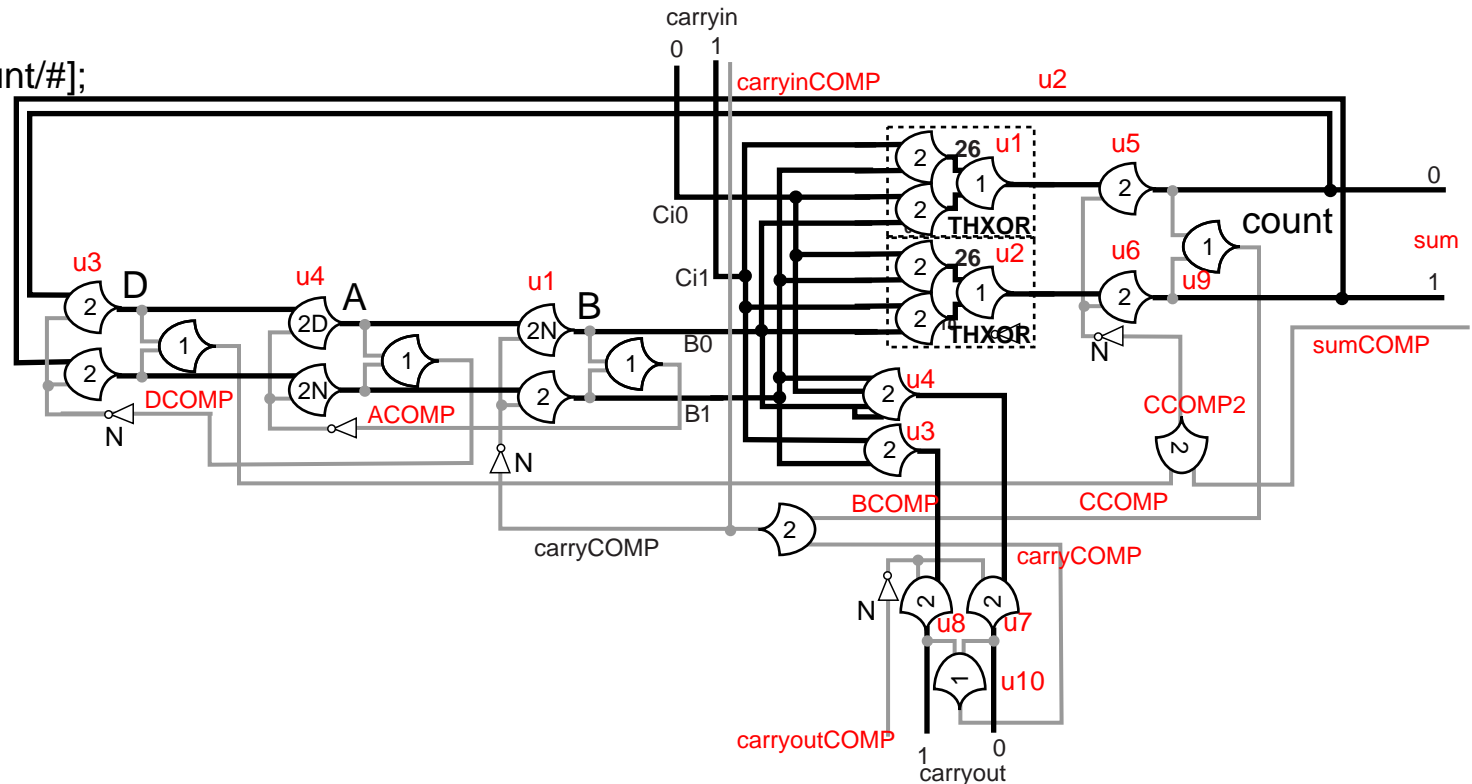

Red names indicate correspondences in the verilog code

twoD-counter_ringA.v
twoD-counter_ringB.v
twoD-counter_ringC.v

Canonical composition


direct mapping from
symbolic specification

Symbolic specification





```
// sink the flow path
(count -> ){
flow count -> ;
token count[0:31]{0:1};
path count/i <
  (count/i -> );
>
}
```

```
// compose the flow path
counter(-> count){
flow -> count;
token count[0:31]{0:1};
token carry[0:32]{0:1};
path count/i <
  (1 -> carry/0);
  digit_count(carry/i -> count/i, carry/i+1)
  (carry/max(i)+1 -> );
>
close count <- ?/#;
}
```

constant 1
component

 


sink
component

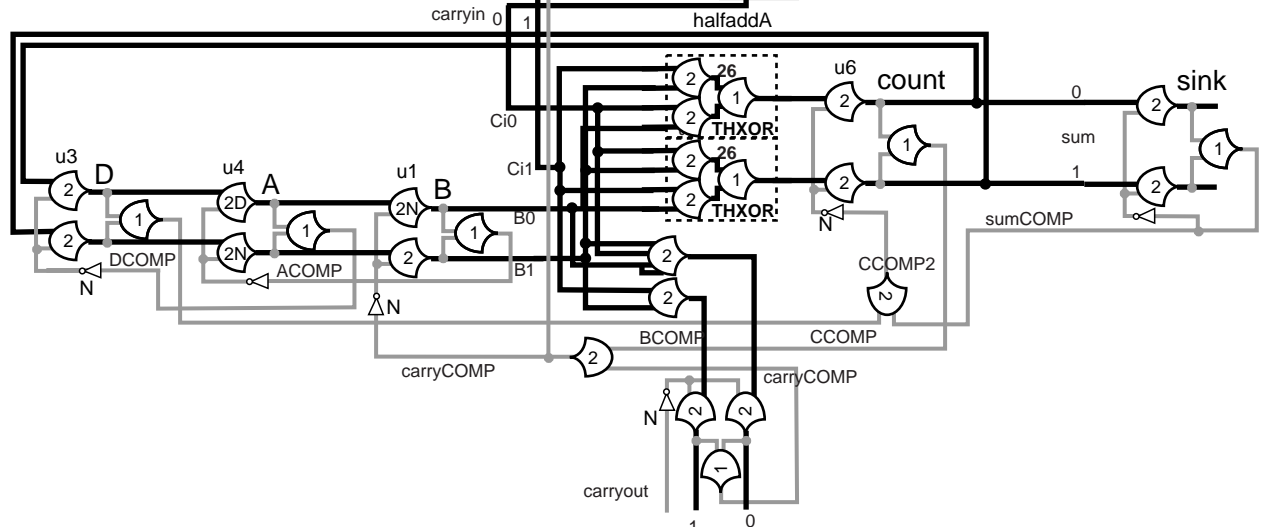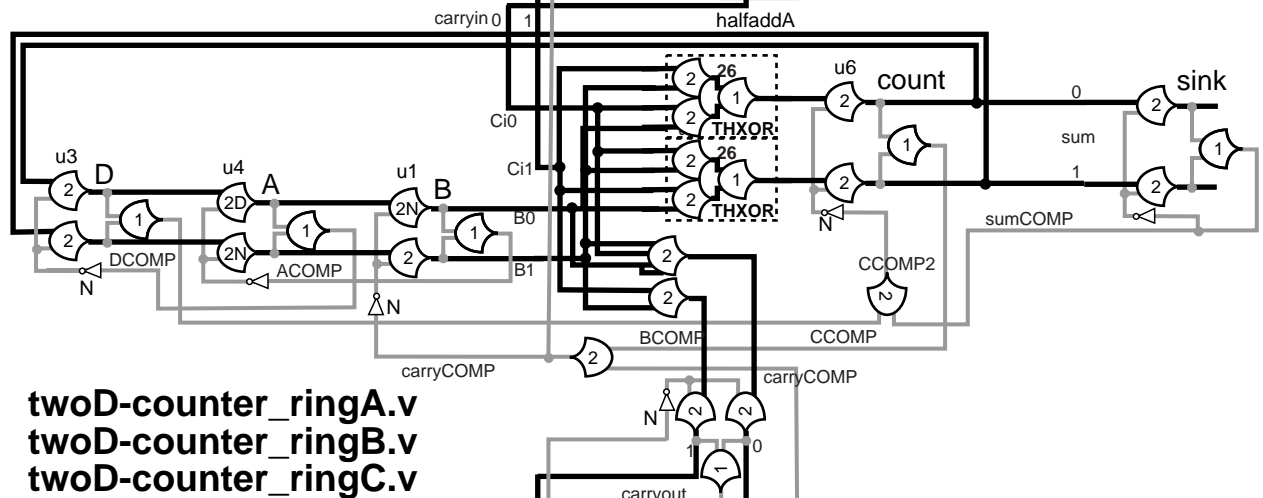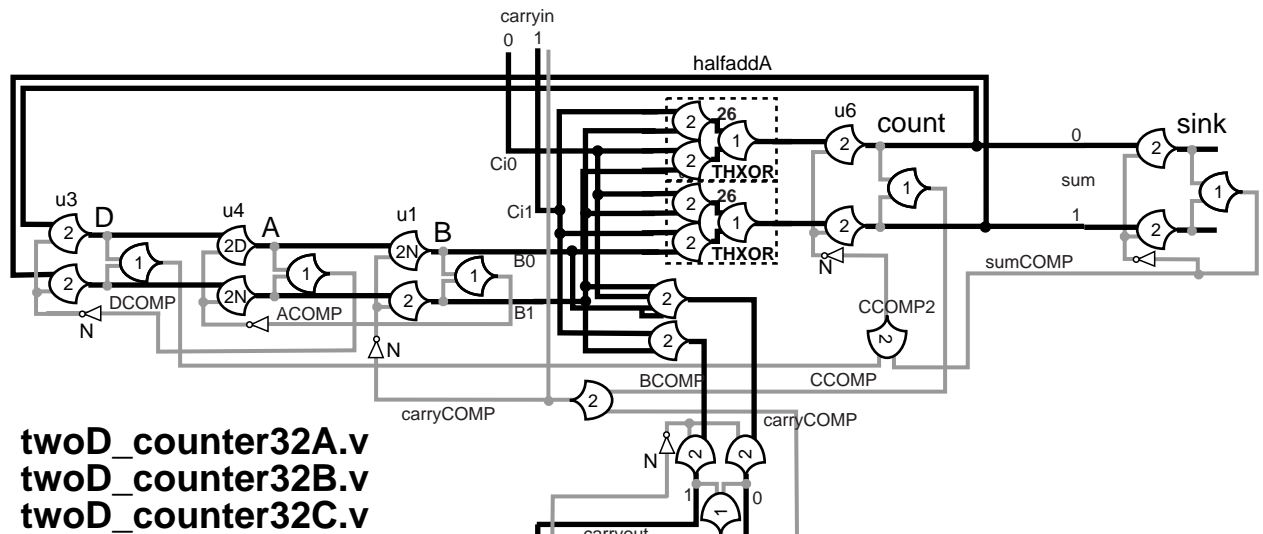 

Cost reduction of carry pipeline

digit_counter32A.v
digit_counter32B.v

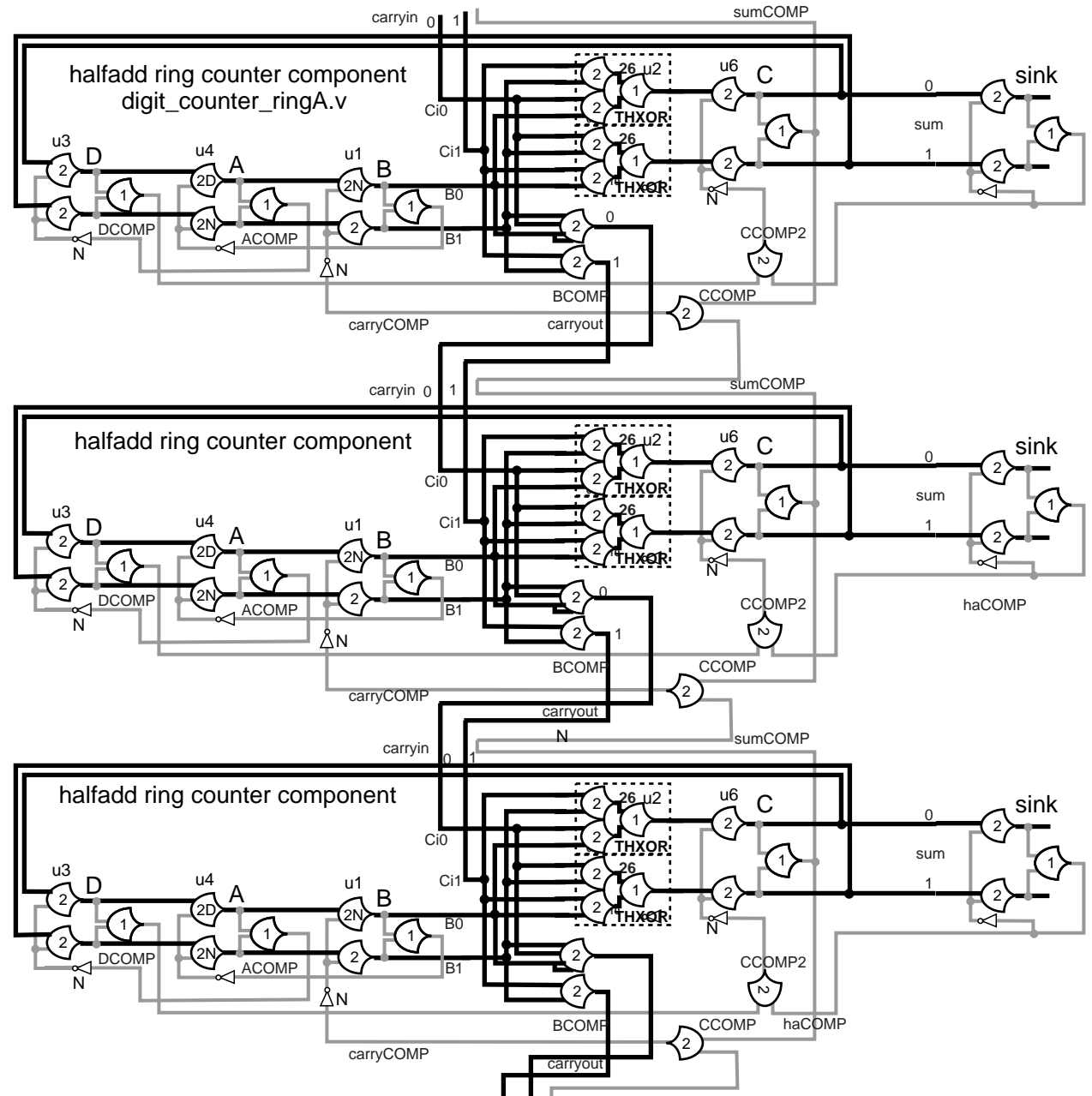digit-counter_ringA.v
digit-counter_ringB.v



Imposition of full token completeness

fullword_counter32A.v
fullword_counter32B.v


fullword-counter_ringA.v
fullword-counter_ringB.v

The flowing wavefronts will conform to whatever logical constraint is imposed

```


counter( -> count){
flow -> count;
token count[0:31]{0:1};
token carry[0:32]{0:1};
path count/i <
  (1 -> carry/0);
  digit_count(carry/i -> count/i, carry/i+1)
  (carry/max(i)+1 -> ));
>
close count <- ?/#;
}
  
```

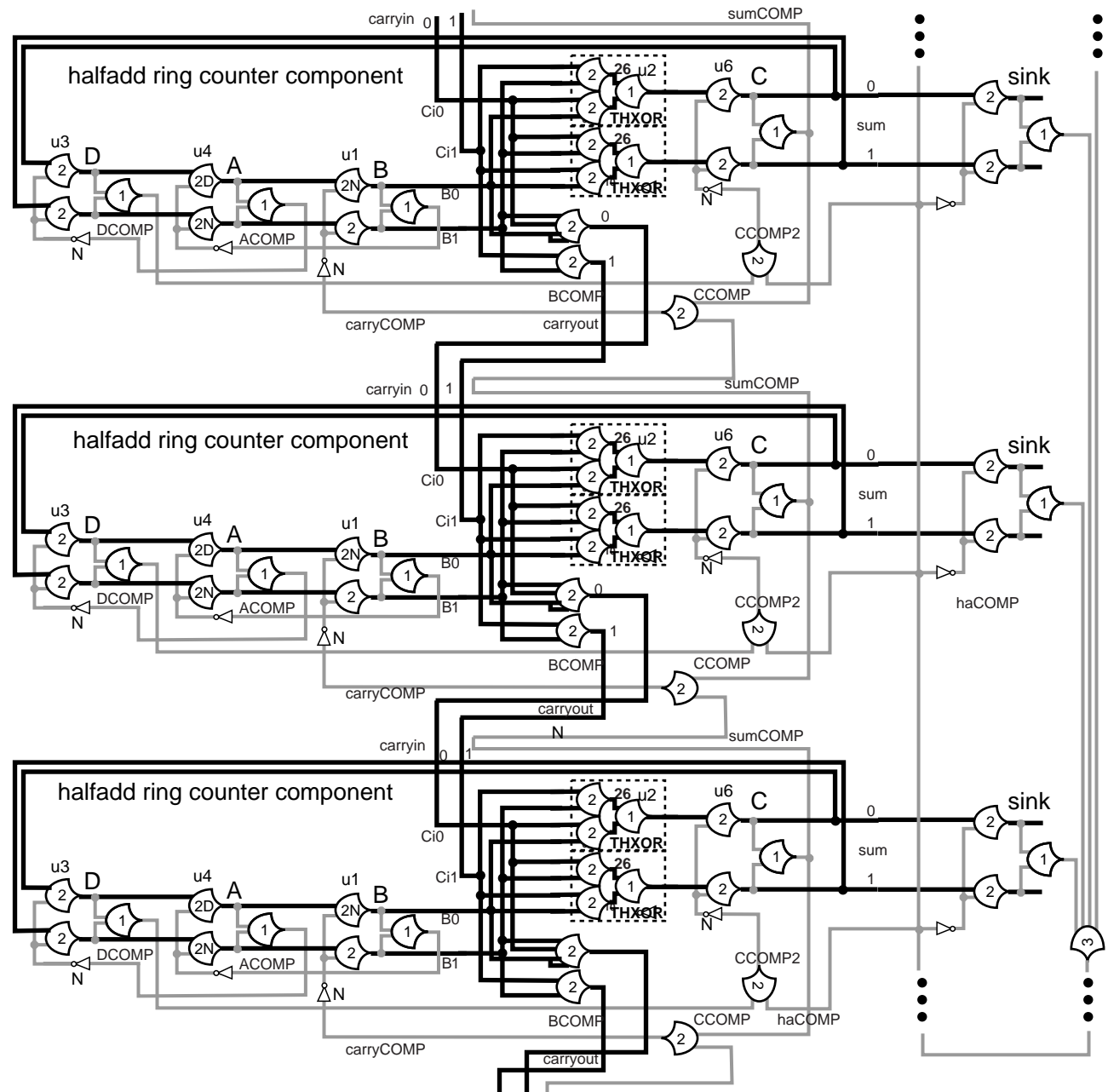Close count <- ?/# specifies that the complete token has to be closed each oscillation but it does not specify how the closure must occur.




Fully integrated combinational logic

 
No gate in the circuit is performing solely combination service. Every gate in the circuit is performing flow coordination duty and a few are also performing combinational duty.



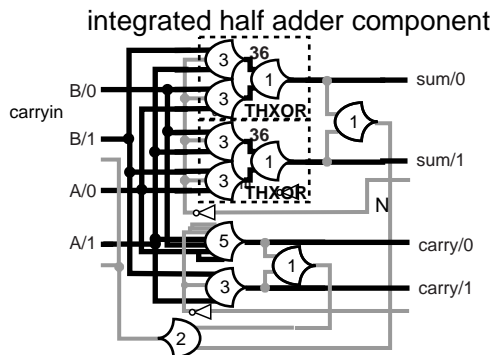A long delay gate creates a long period oscillation which paces the rest of the circuit. Consequently it is slower than the non integrated circuit. But it is fewer gates.




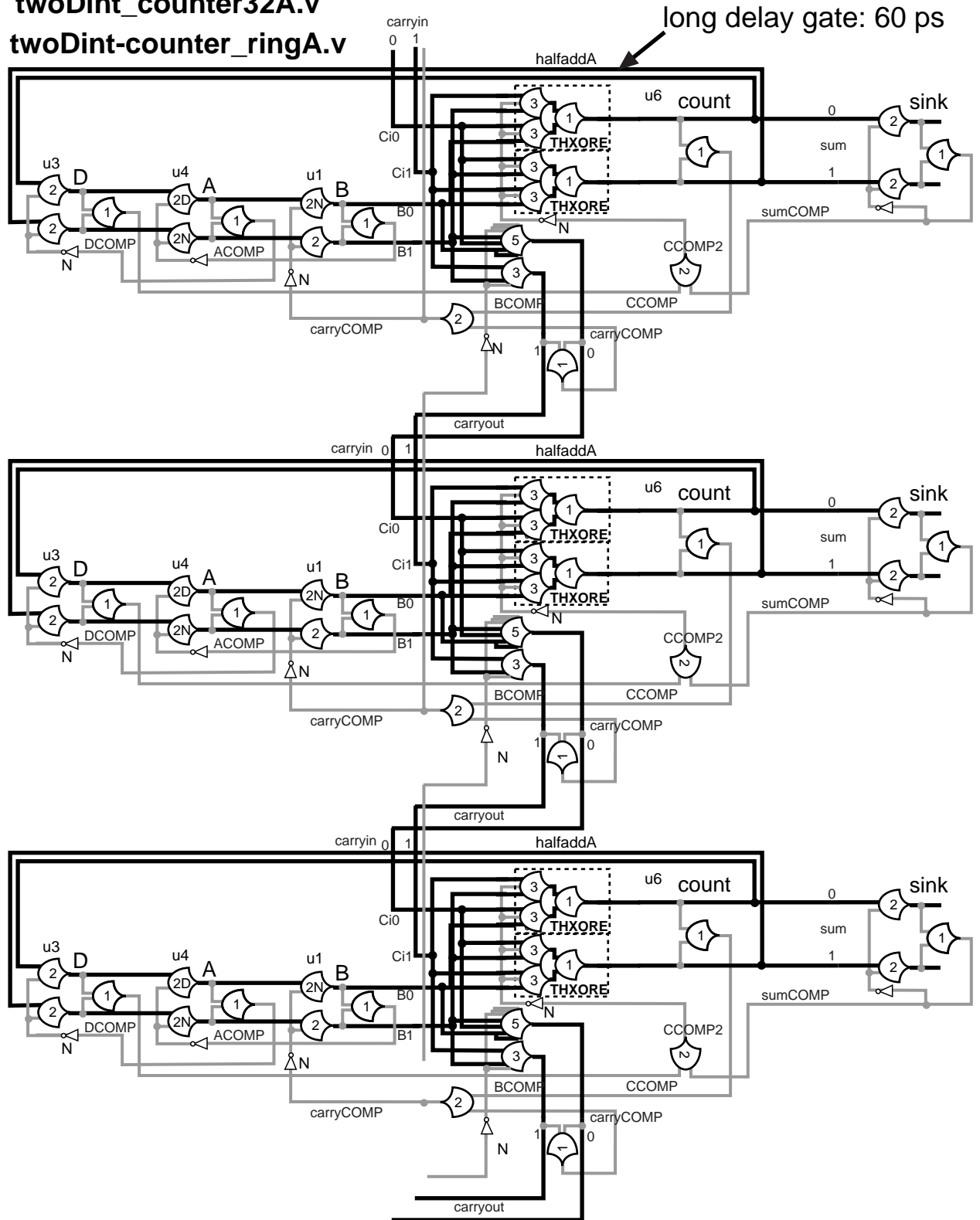twoDint_counter32A.v
twoDint-counter_ringA.v




Fully integrated combinational logic

 No gate in the circuit is performing solely combination service. Every gate in the circuit is performing flow coordination duty and a few are also performing combinational duty.



 The combinational work is distributed over two oscillations with shorter periods. The circuit as a whole flows faster, but it has more gates and more transitions.



twoDint_counter32C.v
twoDint_counter_ringC.v

shorter delay gate: 2 oscillations

