

Presentation Slides

Appendix B Playing With NCL

Logically Determined Design: Clockless System Design With NULL Convention Logic

by Karl Fant


John Wiley & Sons, Inc.

How to implement NCL in FPGAs

Method One

Map NCL gates to Boolean SR flip flop circuits
The resulting Boolean net list is mapped into the FPGA



5. $AB + BC + AC$

 

a. 2of3 operator


Transition to DATA
Transition to NULL

11. $ABC + ABD + ACD + BCD$

  

b. 3of4 operator



3. AB

 

a. 2of2 operator

Transition to DATA
Transition to NULL

6. ABC

  

b. 3of3 operator




Method One

Initialization to DATA or to NULL

5. $AB + BC + AC$



5. $AB + BC + AC$

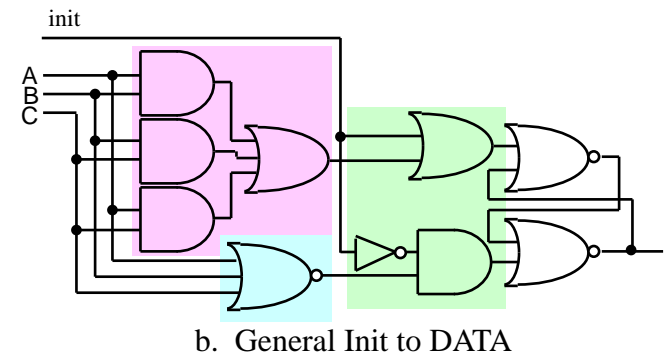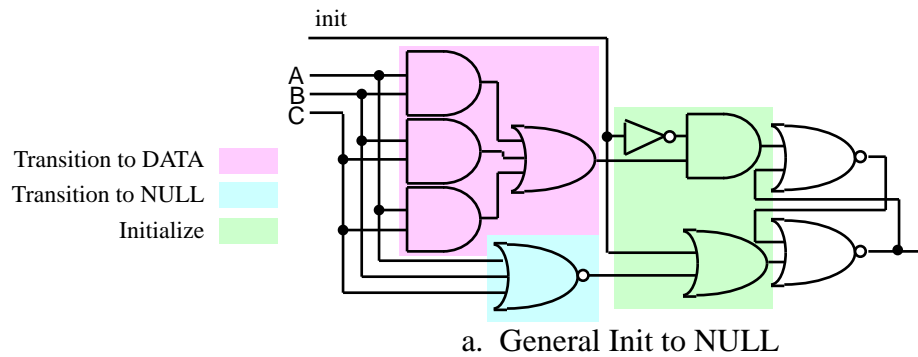 

5. $AB + BC + AC$






3. AB



   3. AB




Transition to DATA
 Transition to NULL
 Initialize




Method One

More examples


 


2. $A + B$

 



a. 1of2 operator

4. $A + B + C$

  



b. 1of3 operator

9. $A + B + C + D$

  



c. 1of4 operator

4. $A + B + C$

  

a. Init to DATA

4. $A + B + C$

  

b. Init to NULL

Initialize

Method Two

Define the NCL gates with logical control

2 of 3 gate

```
module TH23(Z, A, B, C);
output Z; input A; input B; input C;
logic zi;
always @(A or B or C)
begin
if ((A & B) | (A & C) | (B & C))
begin #1 zi <= 1; end
else if ((A==0) & (B==0) & (C==0))
begin #1 zi <= 0; end
end
assign #40 Z = zi;
endmodule
```






Initialize to DATA

```
module TH22D(Z, A, B, I);
output Z; input A; input B; input I;
logic zi;
always @(A or B or I)
begin
if (I == 1)
begin #1 zi <= 1; end
else
if (((A) & (B)))
begin #1 zi <= 1; end
else if (((A==0) & (B==0)))
begin #1 zi <= 0; end
end
assign #40 Z = zi;
endmodule
```

Method Three


FPGA look-up tables can be directly configured to function as Null Convention Logic (NCL) threshold gates.

Look Up Table Configuration and Behavior

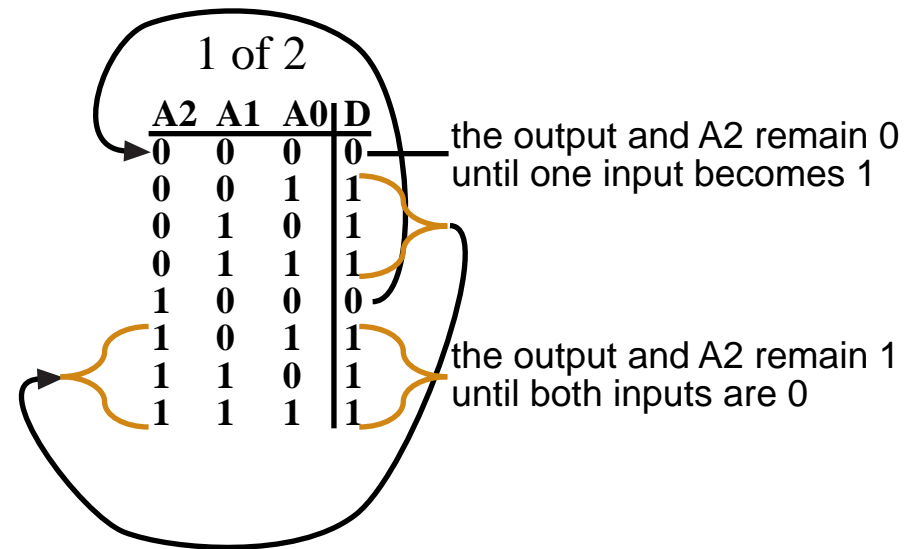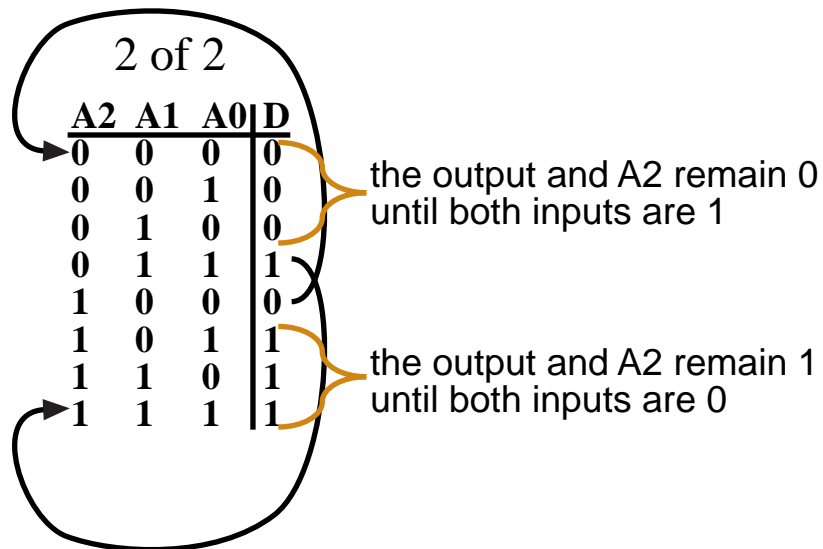   

The LUT Feedback Time Relation

 
As with any NCL gate the feedback in the gate has to be faster than the path around the cycle



2 of 2


A2	A1	A0	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

The cycle path back to A0

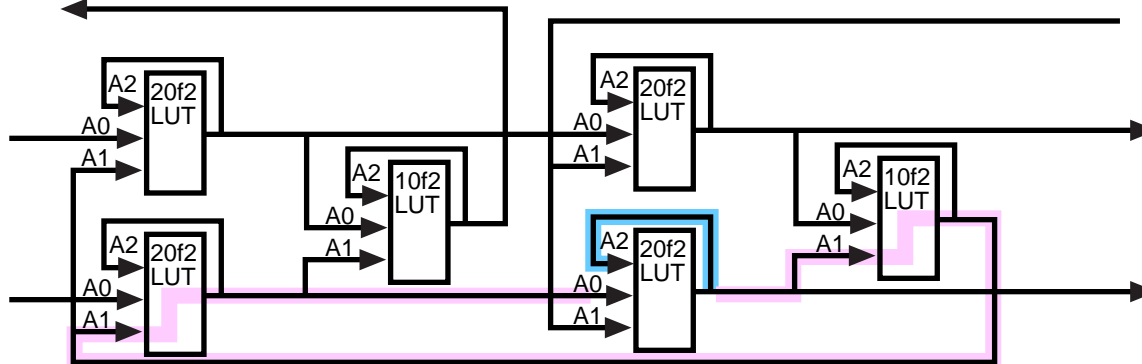

From the branch the blue path has to be faster than the pink path

The cycle path back to A1

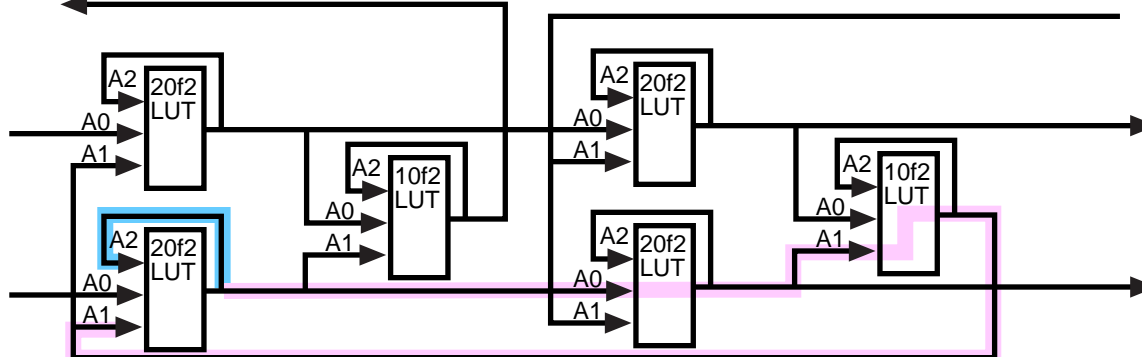


From the branch the blue path has to be faster than the pink path

1 of 2


A2	A1	A0	D
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

2 of 3

 

A3	A2	A1	A0	D
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


2 of 2 in
4 input LUT

 

A3	A2	A1	A0	D
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


A2 is tied to 0 so the effective mapping is in the A2 = 0 sectors. The A2 = 1 sectors are never addressed.

3 of 3

 


A3	A2	A1	A0	D
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

4 of 4

 

A4	A3	A2	A1	A0	D
0	0	0	0	0	0
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	0	1	0
0	0	1	1	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	0	1	0
0	1	0	1	0	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	0
0	1	1	1	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	0	1	1
1	0	0	1	0	1
1	0	0	1	1	1
1	0	1	0	0	1
1	0	1	0	1	1
1	0	1	1	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	1
1	1	0	1	0	1
1	1	0	1	1	1
1	1	1	0	0	1
1	1	1	0	1	1
1	1	1	1	0	1
1	1	1	1	1	1

3 of 5 w2

 


A3 is the weight 2 input.


A4	A3	A2	A1	A0	D
0	0	0	0	0	0
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	0	1	0
0	0	1	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	0	1	1
1	0	0	1	0	1
1	0	0	1	1	1
1	0	1	0	0	1
1	0	1	0	1	1
1	0	1	1	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	1
1	1	0	1	0	1
1	1	0	1	1	1
1	1	1	0	0	1
1	1	1	0	1	1
1	1	1	1	0	1
1	1	1	1	1	1

Initialized Gates

2 of 2 active high init to 1

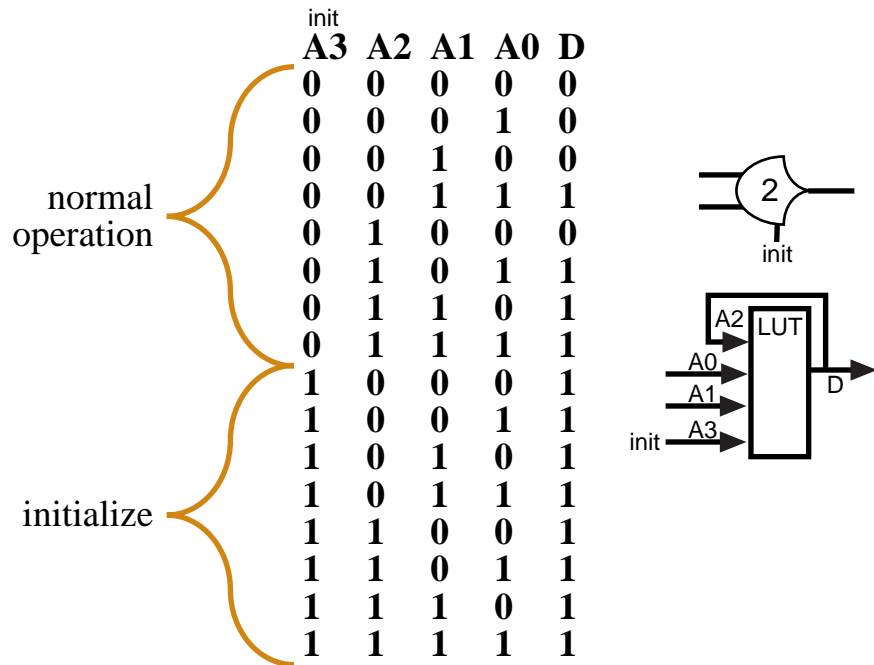

2 of 2 active low init to 0

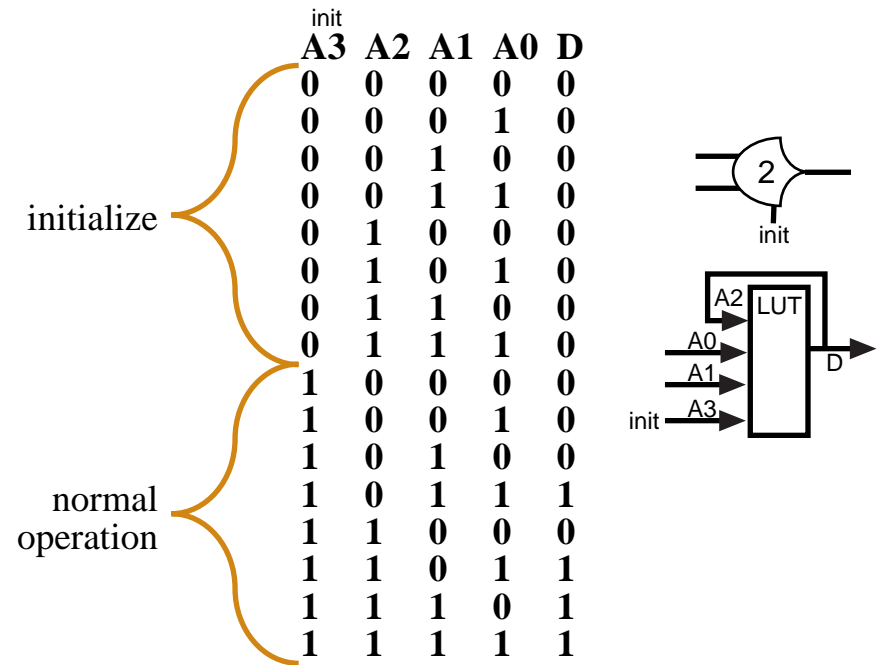

This page intentionally blank

This page intentionally blank